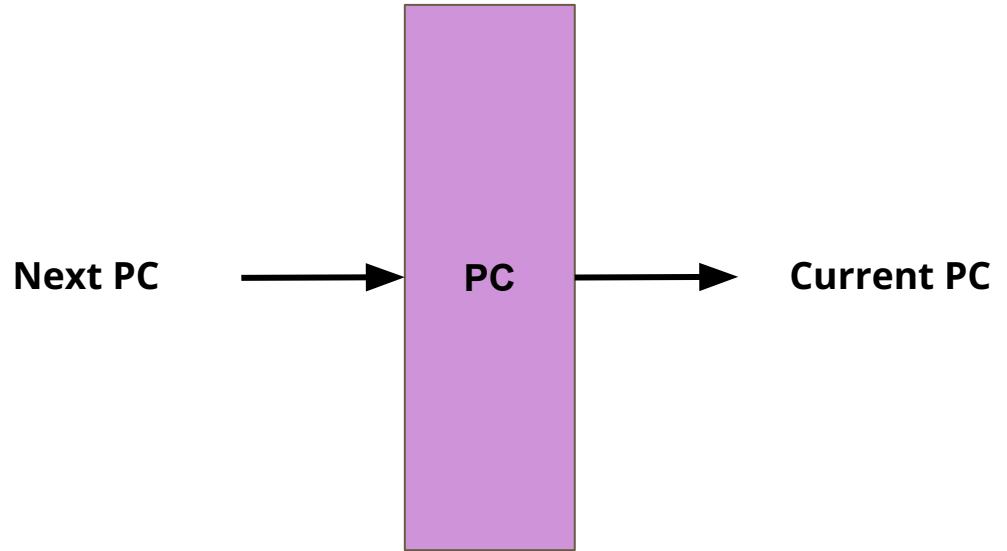

Bits of Architecture

— Basic Processor Design —

What Do We Need to Build a Processor?


Program Counter

- How do we keep track of where we are in our program?
- Input
 - Next PC
- Output
 - Current PC




Instruction Memory

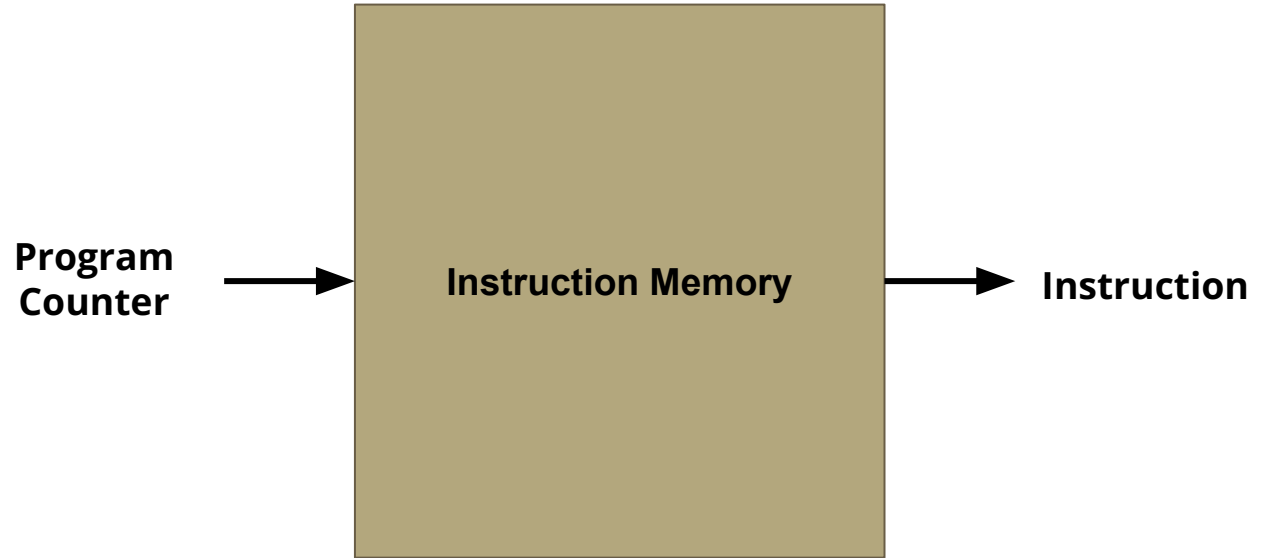- Where do we keep our programs?
- Input
 - Program Counter
- Output
 - Instruction




Registers

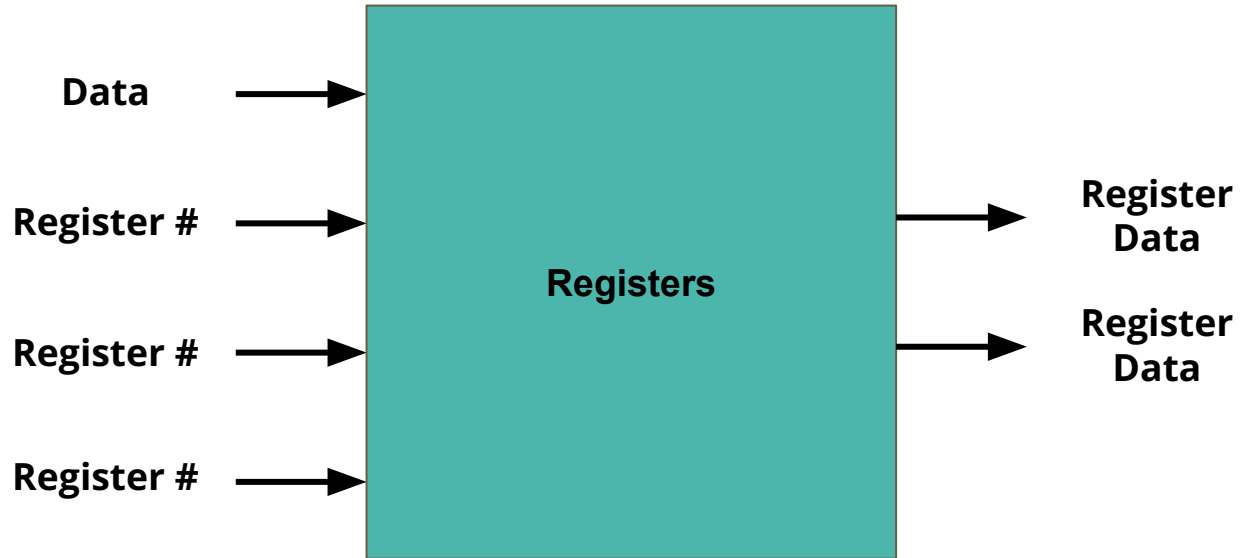- Where do we store the data that our instructions operate on?
- Inputs
 - Register operand(s)
 - Register destination
 - Data
- Output
 - Register data




Data Memory

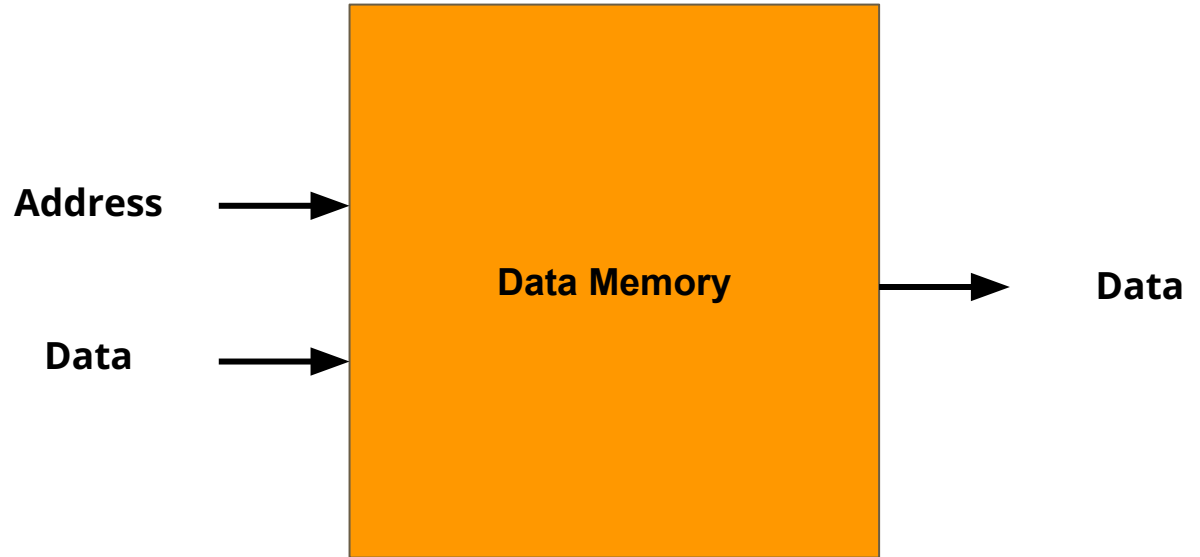- Where is the majority of our data stored?
- Inputs
 - Address
 - Data (Store)
- Output
 - Data read from memory




Arithmetic Logic Unit (ALU)

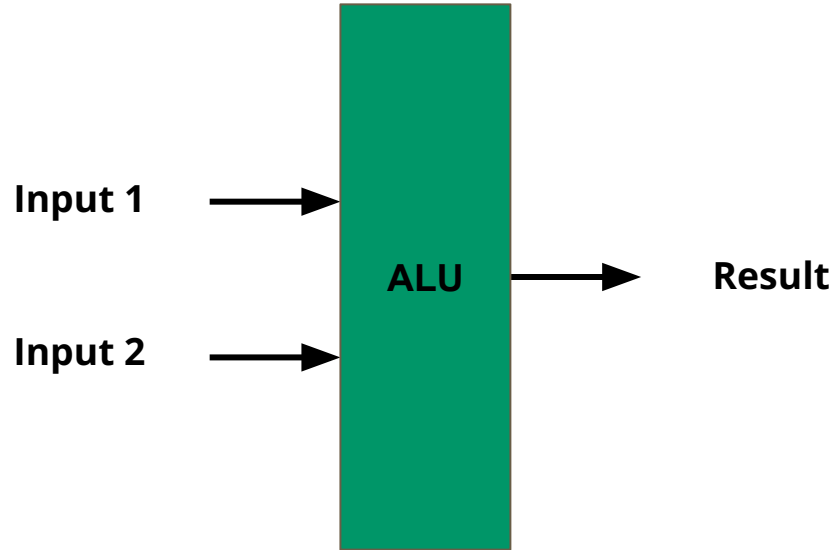- How do we perform arithmetic operations?
 - Manipulate internal state
 - Modify register data
- Inputs
 - Input 1
 - Input 2
- Outputs
 - Result



Multiplexor (Mux)

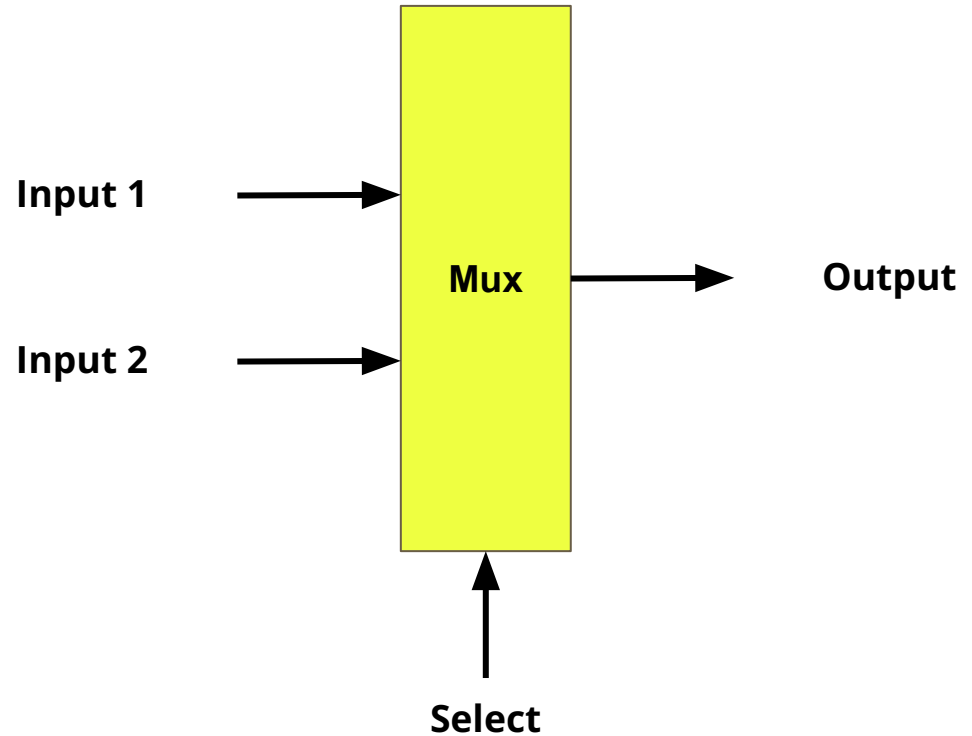
- How do select between different inputs?
- Inputs
 - Input 1
 - Input 2
 - Select
- Output
 - Output



But Wait - Aren't We Forgetting Something?

Control Signals

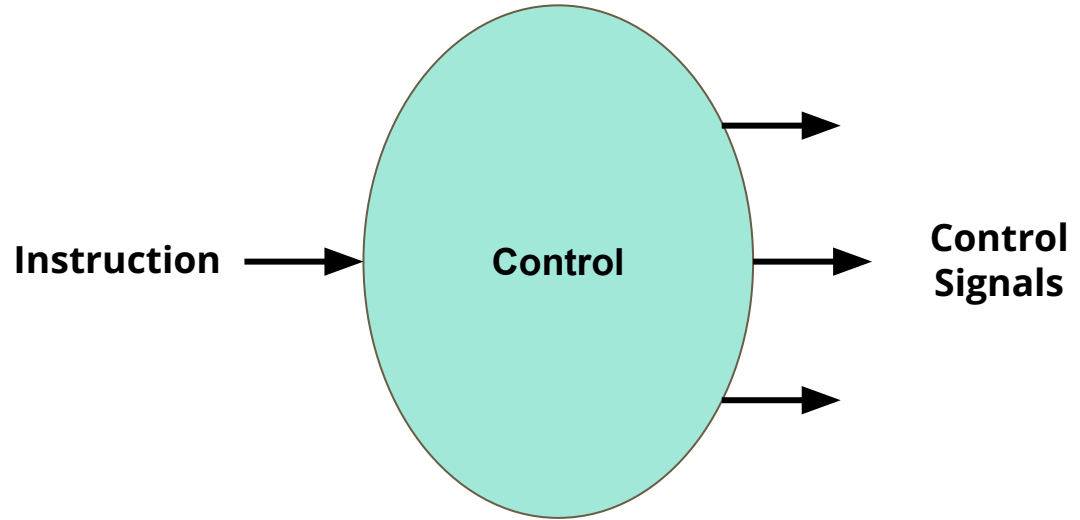- How do we tell our components what to do?
- Control signals
 - Based on instruction
- Examples
 - What operation should an ALU perform?
 - Are we doing a read/write?
 - Mux select lines



Putting it All Together

